

CprE 381

Project Part 1 Report

Lab Partners Vishal Joel and Daniel Limanowski

Section/Lab Time B/Thurs @ 10AM


NOTE: Shane told us in class that we would NOT be docked points for a late submission as we just had to include an extra screenshot for the final part and resubmit.

- a. [Part 0] With your project group members, create a list of best practices / tips for designing, compiling, and testing VHDL modules based on your experiences so far with these labs, both working individually and as a group.
 - Using comments on code that may not be straightforward - Liberal comments are mandatory to maintain reusable code.
 - Proper indentation to ensure readability and reuse. (1 tab indents)
 - Naming convention: All lowercase names with underscores, for readability and name delimiting.
 - Naming convention: Signals should be named using 's_' -> s_signal
- b. [Part 1 (a)] Describe the difference between logical (srl) and arithmetic (sra) shifts. Why does MIPS not have a sla instruction?
 - The purpose of sra is to support signed numbers represented in two's complement. The most significant bit, which is '1' if the value is negative, is duplicated when shifted right. MIPS does not have an sla instruction because a left-shift arithmetic would shift in zeroes from the LSB - this would be the exact same maneuver as a sll, making sla unnecessary.
- c. [Part 1 (b)] In your writeup, briefly describe how your VHDL code implements both the arithmetic and logical shifting operations.
 - The VHDL code uses a "with-select" operation to set a "shift bit" if the inputted "type" bit is set to "0" (logical) or "1" (arithmetic). If logical, "shift bit" is set to "0". If arithmetic, "shift bit" is set to the most-significant-bit (MSB) of the inputted data.
- d. [Part 1 (c)] In your writeup, explain how the right barrel shifter from part b) can be enhanced to also support left shifting operations.
 - The operation of the right barrel shifter need not be altered. A 2-1 multiplexer can be placed in front of the right shifter with a direction bit as the selector. The two inputs to the multiplexer would be 1) the normal input data to be shifted and 2)


the inputted data in REVERSE order. This reversing would require another module to be built that is simply a for loop that swaps all the positions in the input vector. data(31) becomes reverse_data(0) and so on. If a left-shift is desired, the selector chooses the reversed data to be inputted to the right-shift module. After the shift is performed, the left-shift data is reversed one more time to bring it to proper order.

 - e. [Part 1 (d)] Describe how the execution of the different shifting operations corresponds to the Modelsim waveforms in your writeup.


Shift-right-logical (SRL) shifts in zeroes from MSB while moving the data towards LSB.



 Shift-right-arithmetic (SRA) shifts in whatever the MSB is while moving data towards LSB.



 
Shift-left-logical (SLL) shifts in zeroes from the LSB while moving data towards MSB.



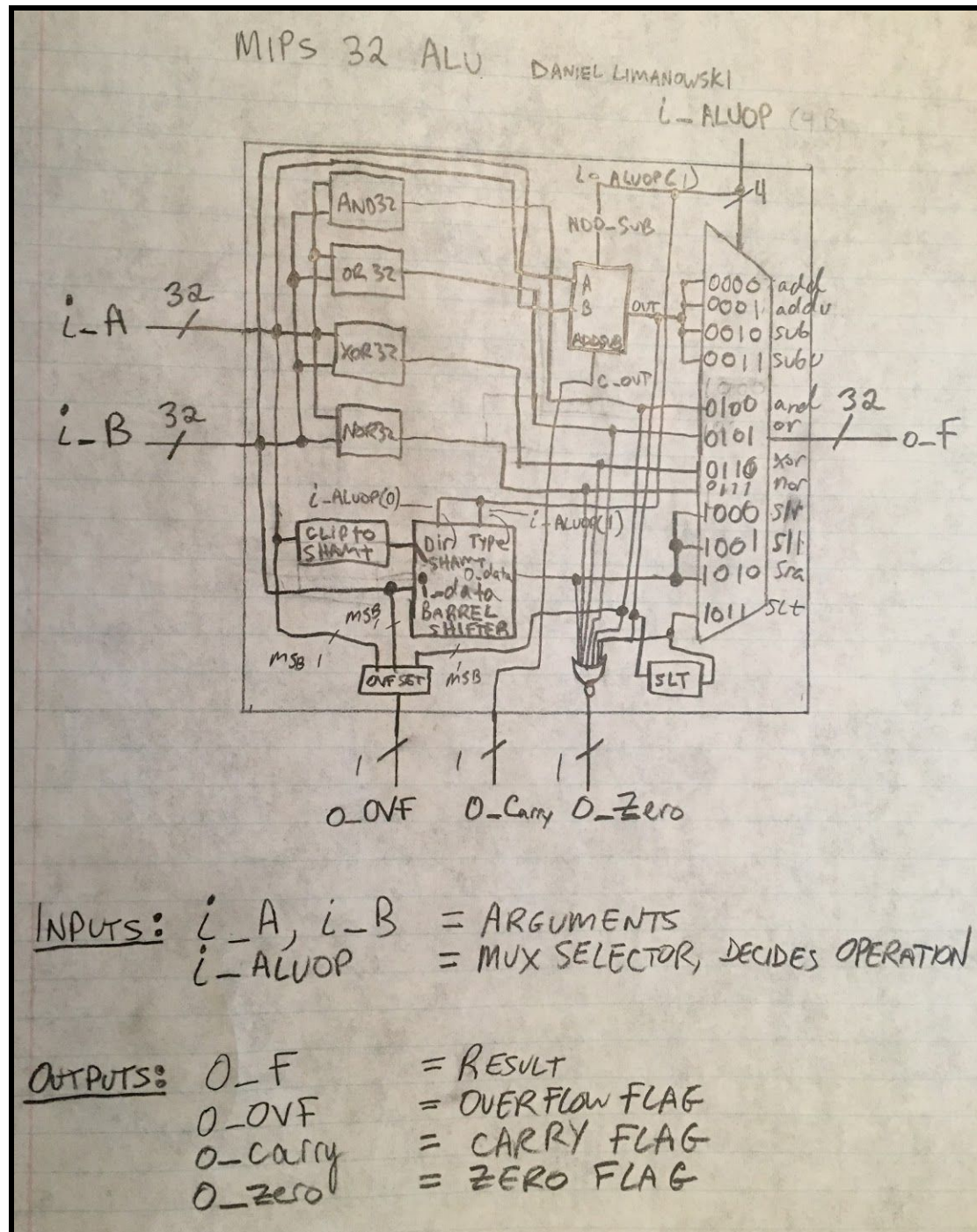- f. [Part 2 (a)] Draw a simplified schematic for this 32-bit ALU. Consider the following questions: how is Overflow calculated? How is Zero calculated? How is slt implemented?

- SLT implementation: Set-less-than instruction is implemented by checking if the result of (a - b) is negative. If negative, (a < b) is true, so we set the LSB of Result (Result(0)) to '1'. If (a-b) is positive, we set Result(0) = '0'. All other bits of Result (ie., 1..31) are always set to '0' regardless. A Less input is added to each 1-bit ALU and for ALU1-30, the Less input is forced to '0'. ALU0's Less is set to ALU31's Set output.

- Zero is calculated by checking all inputs to our ALUOP mux. If any of these inputs are greater than zero, the Zero flag is set to off. If ALL of these inputs are zero, the zero flag is set to on. Using a NOR with the mux inputs as input, the output is our zero flag value.
- Overflow is detected by checking the values of MSB of A, B, and Result of Add/Sub. If (the MSB of A = B) AND (the MSB of Result != (A or B's MSB)), then set Overflow flag. Overflow (OVF) is ONLY looked at in SIGNED operations (add, sub).
- 32-bit ALU simple schematic (NOTE: ALUOPcodes have changed. See Mux7-1 file for current opcodes):




g. [Part 2 (b)] In your writeup, describe what challenges (if any) you faced in implementing this module.


Wrapping my head around the entire ALU unit, with all of its operations, was a challenge. However, once I drew in detail the ALU and all of the components needed to implement it, actually writing the VHDL code wasn't all that bad. Office hours were a good assist in understanding what was expected from the ALU and how to get started.

 - h. [Part 2 (c)] Describe how the execution of the different operations corresponds to the Modelsim waveforms in your writeup.


ALUOP for Add = 0b0010. We added 0+0 and the result was 0. You can see the Zero flag is properly set in the figure below.



 
ALUOP for Sub = 0b0110. We subtracted 0b010 from 0b110 and obtained 0b100.



 ALUOP for SRL is 0b1000. SHAMT (shift amount) is i_A, set to shift right 5 bits. The register data to shift is i_B, a lonely bit in a sea of 31 zeroes. You can tell the bit is properly shifted right 5 bits.




 ALUOP for SLT is 0b0111. First we set A<B and see the answer is 1 (correct). Then we set A>B and see the result is also correct (= 0).




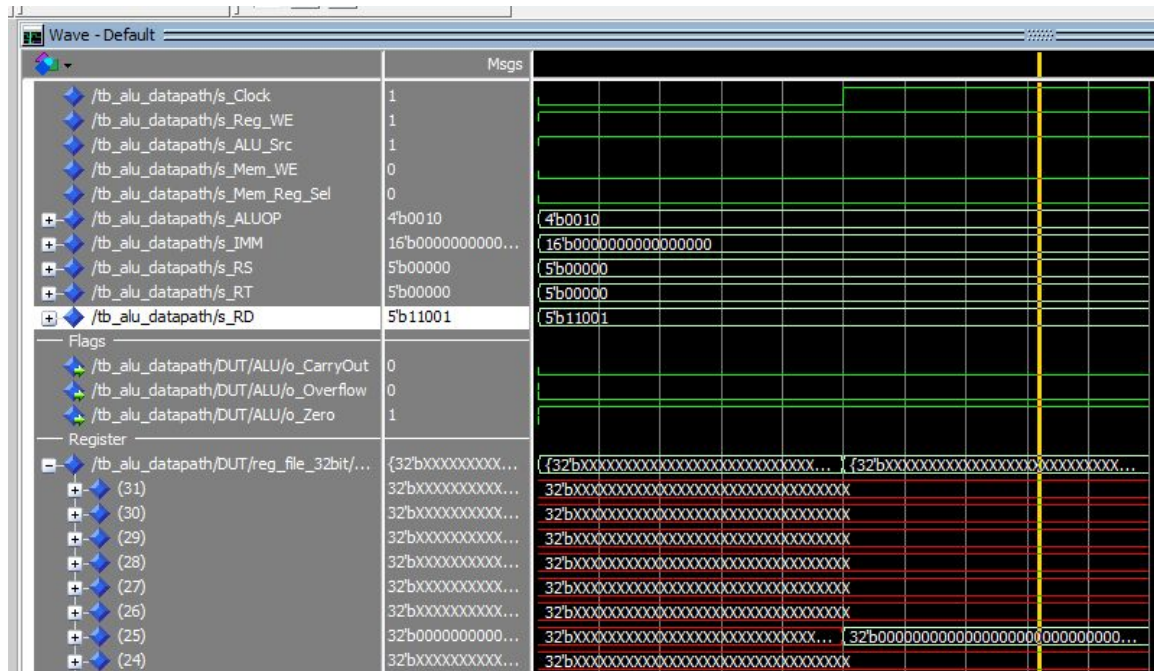- i. [Part 3(b)] justify why your test plan is comprehensive. Include waveforms that demonstrate your test programs functioning.

Our test plan is comprehensive because I developed a testbench to ensure accuracy for all the possible commands. I have included in the report a few screenshots from my tests.



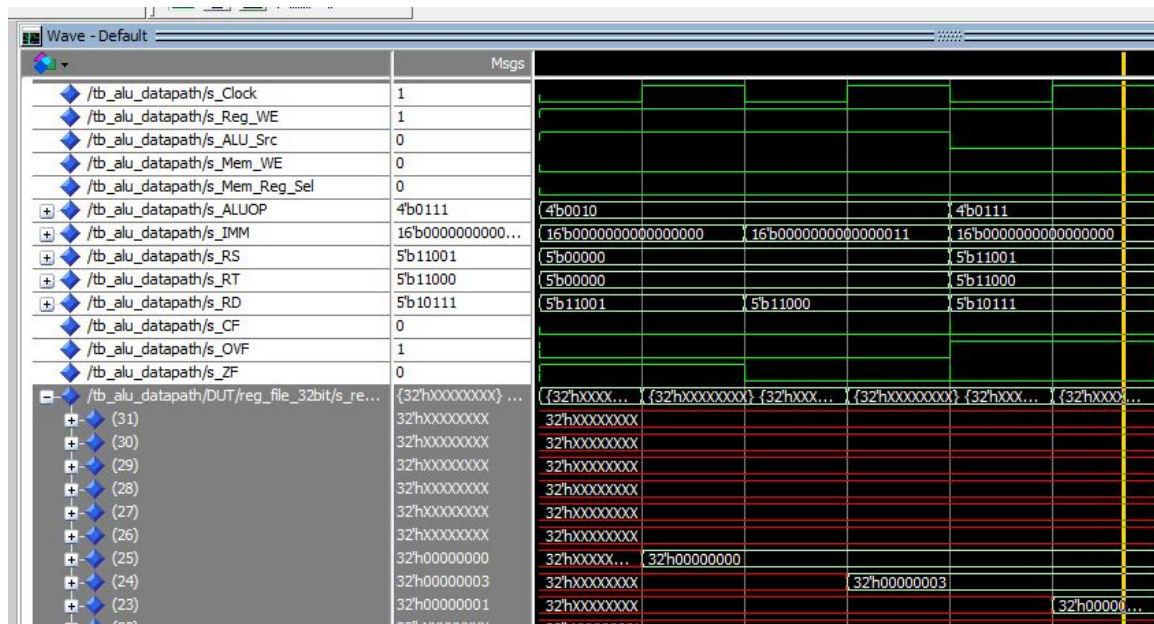The figure above shows addition of the zero register with an immediate “0”. The ALUOP for addition is “0010” as seen in the waveform.



The above image shows the SLT operation in working condition. We compare register 25 (holding a value of 0) to register 24 (holding a value of 3). 3 is clearly greater than 0, so SLT is set to 1 (whose result is placed into \$23, as seen in the waveform).

- j. [Part 4(d)] Does your design meet the timing constraints that were set? Report the critical path from register to register using TimeQuest. What is the fastest clock period that your MIPS datapath can be safely run at?

To implement a 50 MHz clock, the period was set to 20 ns and the rise was set to 10 ns.

Our design did NOT meet the timing constraints (50 MHz clock) that were set. We had a negative slack (at worst) of -11.67 ns.

Our highest “slack” value was -11.767 nanoseconds (ns) for the flip flops located inside of the register file. This is our limiting factor in terms of speed. A negative slack indicates that our slack went OVER the clock period. Instead of completing the critical path within 20 ns, we took 31.767 ns in our worst-case.

The fastest clock period we can run our datapath at is 31 MHz.

Below shows the critical path:

	Location	Element	Partition	Bounding Box	Local Const Source
1	FF_X83_Y26_N13	reg_file_32bit\genera...NFOR:5:flip_flop s_Q q	Top	n/a	n/a
2	LCCOMB_X84_Y29_N16	reg_file_32bit mux_RD2 Mux26~12 datad	Top	n/a	n/a
3	LCCOMB_X84_Y29_N10	reg_file_32bit mux_RD2 Mux26~13 datad	Top	n/a	n/a
4	LCCOMB_X83_Y31_N18	reg_file_32bit mux_RD2 Mux26~14 datad	Top	n/a	n/a
5	LCCOMB_X83_Y31_N8	reg_file_32bit mux_RD2 Mux26~15 datad	Top	n/a	n/a
6	LCCOMB_X81_Y29_N0	reg_file_32bit mux_RD2 Mux26~16 datad	Top	n/a	n/a
7	LCCOMB_X80_Y32_N28	reg_file_32bit mux_RD2 Mux26~19 datad	Top	n/a	n/a
8	LCCOMB_X80_Y32_N26	imm_or_reg \GENFOR:5:or_xysel o_F~0 datad	Top	n/a	n/a
9	LCCOMB_X80_Y32_N14	ALU ARITH_OP adder \GENFOR:5:or_fin o_F~0 datac	Top	n/a	n/a
10	LCCOMB_X81_Y35_N20	ALU ARITH_OP adder \GENFOR:6:or_fin o_F~0 datad	Top	n/a	n/a
11	LCCOMB_X81_Y35_N2	ALU ARITH_OP adder \GENFOR:7:or_fin o_F~0 datad	Top	n/a	n/a
12	LCCOMB_X81_Y35_N24	ALU ARITH_OP adder \GENFOR:8:or_fin o_F~0 datad	Top	n/a	n/a
13	LCCOMB_X81_Y35_N30	ALU ARITH_OP adder \GENFOR:9:or_fin o_F~0 datad	Top	n/a	n/a
14	LCCOMB_X81_Y35_N0	ALU ARITH_OP adder \GENFOR:10:or_fin o_F~0 datac	Top	n/a	n/a
15	LCCOMB_X81_Y35_N10	ALU ARITH_OP adder \GENFOR:11:or_fin o_F~0 datad	Top	n/a	n/a
16	LCCOMB_X81_Y35_N16	ALU ARITH_OP adder \GENFOR:12:or_fin o_F~0 datad	Top	n/a	n/a
17	LCCOMB_X81_Y35_N6	ALU ARITH_OP adder \GENFOR:13:or_fin o_F~0 datad	Top	n/a	n/a
18	LCCOMB_X81_Y35_N28	ALU ARITH_OP adder \GENFOR:14:or_fin o_F~0 datad	Top	n/a	n/a
19	LCCOMB_X81_Y35_N18	ALU ARITH_OP adder \GENFOR:15:or_fin o_F~0 datad	Top	n/a	n/a
20	LCCOMB_X81_Y35_N12	ALU ARITH_OP adder \GENFOR:16:or_fin o_F~0 datad	Top	n/a	n/a
21	LCCOMB_X81_Y35_N26	ALU ARITH_OP adder \GENFOR:17:or_fin o_F~0 datad	Top	n/a	n/a
22	LCCOMB_X80_Y35_N16	ALU ARITH_OP adder \GENFOR:18:or_fin o_F~0 datad	Top	n/a	n/a
23	LCCOMB_X80_Y35_N26	ALU ARITH_OP adder \GENFOR:19:or_fin o_F~0 datad	Top	n/a	n/a
24	LCCOMB_X80_Y35_N4	ALU ARITH_OP adder \GENFOR:20:or_fin o_F~0 datac	Top	n/a	n/a
25	LCCOMB_X80_Y35_N2	ALU ARITH_OP adder \GENFOR:21:or_fin o_F~0 datac	Top	n/a	n/a
26	LCCOMB_X80_Y35_N24	ALU ARITH_OP adder \GENFOR:22:or_fin o_F~0 datad	Top	n/a	n/a
27	LCCOMB_X80_Y35_N22	ALU ARITH_OP adder \GENFOR:23:or_fin o_F~0 datad	Top	n/a	n/a
28	LCCOMB_X80_Y35_N12	ALU ARITH_OP adder \GENFOR:24:or_fin o_F~0 datac	Top	n/a	n/a
29	LCCOMB_X80_Y35_N18	ALU ARITH_OP adder \GENFOR:25:or_fin o_F~0 datad	Top	n/a	n/a
30	LCCOMB_X80_Y35_N28	ALU ARITH_OP adder \GENFOR:26:or_fin o_F~0 datad	Top	n/a	n/a
31	LCCOMB_X80_Y35_N10	ALU ARITH_OP adder \GENFOR:27:or_fin o_F~0 datad	Top	n/a	n/a
32	LCCOMB_X80_Y35_N8	ALU ARITH_OP adder \GENFOR:28:or_fin o_F~0 datad	Top	n/a	n/a
33	LCCOMB_X80_Y35_N6	ALU ARITH_OP adder \GENFOR:29:or_fin o_F~0 datac	Top	n/a	n/a
34	LCCOMB_X80_Y35_N20	ALU ARITH_OP adder \GENFOR:30:or_fin o_F~0 datad	Top	n/a	n/a
35	LCCOMB_X80_Y35_N30	ALU SELECT_OPERATION Mux31~8 datad	Top	n/a	n/a
36	LCCOMB_X80_Y35_N0	ALU SELECT_OPERATION Mux31~9 datac	Top	n/a	n/a
37	LCCOMB_X80_Y35_N14	s_convert_to_nat[0]~3 datad	Top	n/a	n/a
38	LCCOMB_X63_Y51_N10	memory_unit ram~42246 datad	Top	n/a	n/a
39	LCCOMB_X63_Y51_N12	memory_unit ram~42249 datad	Top	n/a	n/a
40	LCCOMB_X70_Y48_N22	memory_unit ram~42260 datad	Top	n/a	n/a
41	LCCOMB_X70_Y48_N4	memory_unit ram~42271 datac	Top	n/a	n/a
42	LCCOMB_X70_Y48_N14	memory_unit ram~42314 datac	Top	n/a	n/a
43	LCCOMB_X92_Y32_N26	memory_unit ram~42357 datac	Top	n/a	n/a
44	LCCOMB_X92_Y32_N24	memory_unit ram~42358 dataa	Top	n/a	n/a
45	LCCOMB_X91_Y32_N30	mem_or_reg \GENFOR:18:or_xysel o_F~0 datad	Top	n/a	n/a
46	FF_X84_Y35_N29	reg_file_32bit\genera...8:flip_flop s_Q asdata	Top	n/a	n/a


A general screenshot from the timing window after analysis:

Slack	From Node	To Node	Launch Clock	Latch Clock	Relationship	Clock Skew	Data Delay
1 -11.767	register_file_reg_file_32bit[register_nbit]gen_5[register_32bit][diff_MS]GENFOR:5[flp_flop]s_Q	register_file_reg_file_32bit[register_nbit]gen_...[register_32bit][diff_MS]GENFOR:18[flp_flop]s_Q	l_clock	l_clock	20.000	-0.038	31.727

Path #1: Setup slack is -11.767 (VIOLATED)

Path Summary	Statistics	Data Path	Waveform	Extra Filter Information
26 LCOMB_X80_Y35_N24 ALU[ARITH_OP]adder[GENFOR:22]or_f[no]_f--0[datad] Top	n/a	n/a	n/a	no
27 LCOMB_X80_Y35_N22 ALU[ARITH_OP]adder[GENFOR:22]or_f[no]_f--0[datad] Top	n/a	n/a	n/a	no
28 LCOMB_X80_Y35_N12 ALU[ARITH_OP]adder[GENFOR:24]or_f[no]_f--0[datad] Top	n/a	n/a	n/a	no
29 LCOMB_X80_Y35_N18 ALU[ARITH_OP]adder[GENFOR:23]or_f[no]_f--0[datad] Top	n/a	n/a	n/a	no
30 LCOMB_X80_Y35_N28 ALU[ARITH_OP]adder[GENFOR:26]or_f[no]_f--0[datad] Top	n/a	n/a	n/a	no
31 LCOMB_X80_Y35_N10 ALU[ARITH_OP]adder[GENFOR:27]or_f[no]_f--0[datad] Top	n/a	n/a	n/a	no
32 LCOMB_X80_Y35_N8 ALU[ARITH_OP]adder[GENFOR:28]or_f[no]_f--0[datad] Top	n/a	n/a	n/a	no
33 LCOMB_X80_Y35_N6 ALU[ARITH_OP]adder[GENFOR:29]or_f[no]_f--0[datad] Top	n/a	n/a	n/a	no
34 LCOMB_X80_Y35_N20 ALU[ARITH_OP]adder[GENFOR:30]or_f[no]_f--0[datad] Top	n/a	n/a	n/a	no
35 LCOMB_X80_Y35_N30 ALU[SELECT_OPERATION]Mux31--9[datad] Top	n/a	n/a	n/a	no
36 LCOMB_X80_Y35_N0 ALU[SELECT_OPERATION]Mux31--9[datad] Top	n/a	n/a	n/a	no
37 LCOMB_X80_Y35_N14 s_convert_to_n[0]--0[datad] Top	n/a	n/a	n/a	no
38 LCOMB_X63_Y51_N10 memory_unit[ram--42]6[datad] Top	n/a	n/a	n/a	no
39 LCOMB_X63_Y51_N12 memory_unit[ram--42]49[datad] Top	n/a	n/a	n/a	no
40 LCOMB_X70_Y48_N22 memory_unit[ram--42]60[datad] Top	n/a	n/a	n/a	no
41 LCOMB_X70_Y48_N4 memory_unit[ram--42]71[datad] Top	n/a	n/a	n/a	no
42 LCOMB_X70_Y48_N14 memory_unit[ram--42]14[datad] Top	n/a	n/a	n/a	no
43 LCOMB_X92_Y32_N26 memory_unit[ram--42]37[datad] Top	n/a	n/a	n/a	no
44 LCOMB_X92_Y32_N24 memory_unit[ram--42]35[datad] Top	n/a	n/a	n/a	no
45 LCOMB_X91_Y32_N30 mem_ar_reg[GENFOR:18]or_xy[flp_flop]_f--0[datad] Top	n/a	n/a	n/a	no
46 FF_X84_Y35_N29 reg_file_32bit[genera...8[flp_flop]_Q]asdata Top	n/a	n/a	n/a	no

Graphical Data Path

 

The thumbnail view shows a quick visual representation of the extra filter information related to this path. The path connections appear as heavy black lines. Netlist nodes along the path and routing drivers along the routing path appear as black dots. The routing connections appear as thin black lines. No directional information is shown for path or routing connections. Any bounding boxes listed in Extra Filter Information appear as shaded blue rectangles.

Path #1: Setup slack is -11.767 (VIOLATED)

